

Multivariate Diff Eq II

- * Change of Basis
 - * Diagonalization & Change of Basis
 - * Circuit Examples of Multivariate Diff Eq
 - LC Tank
 - Driven RLC Circuit
- (Worksheet)

I. Change of Basis


Consider $\vec{x}_e = \begin{pmatrix} 0 \\ 1 \end{pmatrix}$

$$\vec{e}_1 = \begin{pmatrix} 1 \\ 0 \end{pmatrix} \quad \vec{e}_2 = \begin{pmatrix} 0 \\ 1 \end{pmatrix}$$

(standard basis)

$$\vec{x}_e = 0\vec{e}_1 + 1\vec{e}_2$$

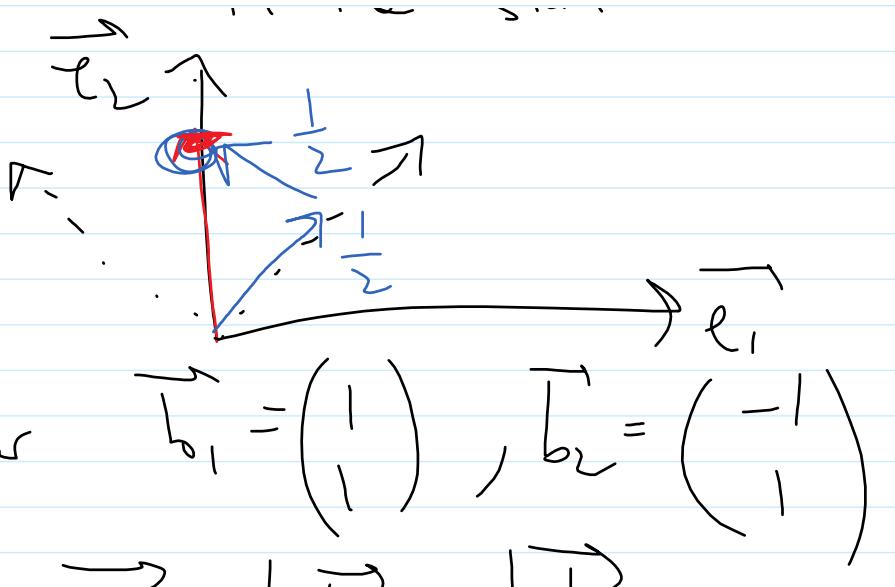$\vec{x}_e = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$ is the coordinates of \vec{x}
in the standard basis
 \vec{e}_1, \vec{e}_2



Consider $\vec{b}_1 = \begin{pmatrix} 1 \\ 1 \end{pmatrix}$, $\vec{b}_2 = \begin{pmatrix} -1 \\ 1 \end{pmatrix}$

$$\vec{x}_e = \frac{1}{2} \vec{b}_1 + \frac{1}{2} \vec{b}_2$$

$\vec{x}_B = \begin{pmatrix} \frac{1}{2} \\ \frac{1}{2} \end{pmatrix}$ is coordinates of \vec{x} in the B basis

Same point, different representation!

How do we relate those 2 representations
 \Rightarrow how to do a "change of basis"

$$\vec{x}_e = \frac{1}{2} \vec{b}_1 + \frac{1}{2} \vec{b}_2 = \begin{pmatrix} \vec{b}_1 & \vec{b}_2 \end{pmatrix} \begin{pmatrix} \frac{1}{2} \\ \frac{1}{2} \end{pmatrix}$$


$$\vec{x}_e = B \vec{x}_B$$

$$\boxed{\vec{x} \rightarrow B^{-1} \cdot \vec{x}}$$

$$\boxed{\vec{x}_b = B^{-1} \vec{x}_e}$$

Change of basis, std \rightarrow B basis

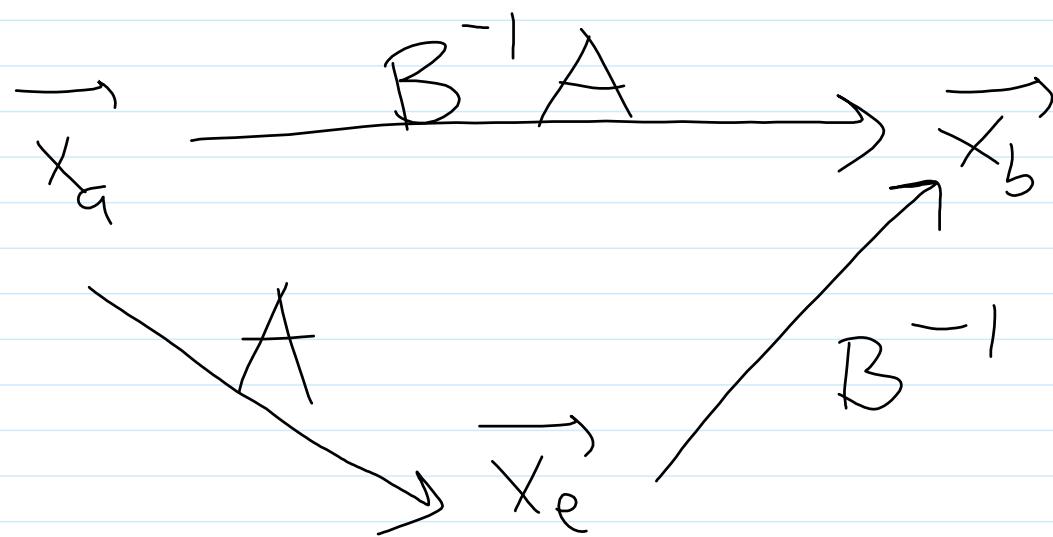How might we change from any basis A (not necessarily std basis) to basis B?



$$\boxed{\vec{x}_b = B^{-1} A \vec{x}_a}$$

$$C_{A \rightarrow B} = B^{-1} A$$

In fact, earlier case is special case.


$$A = I$$

$$C_{A \rightarrow B} = B^{-1} A = B^{-1} I = B^{-1}$$

As before

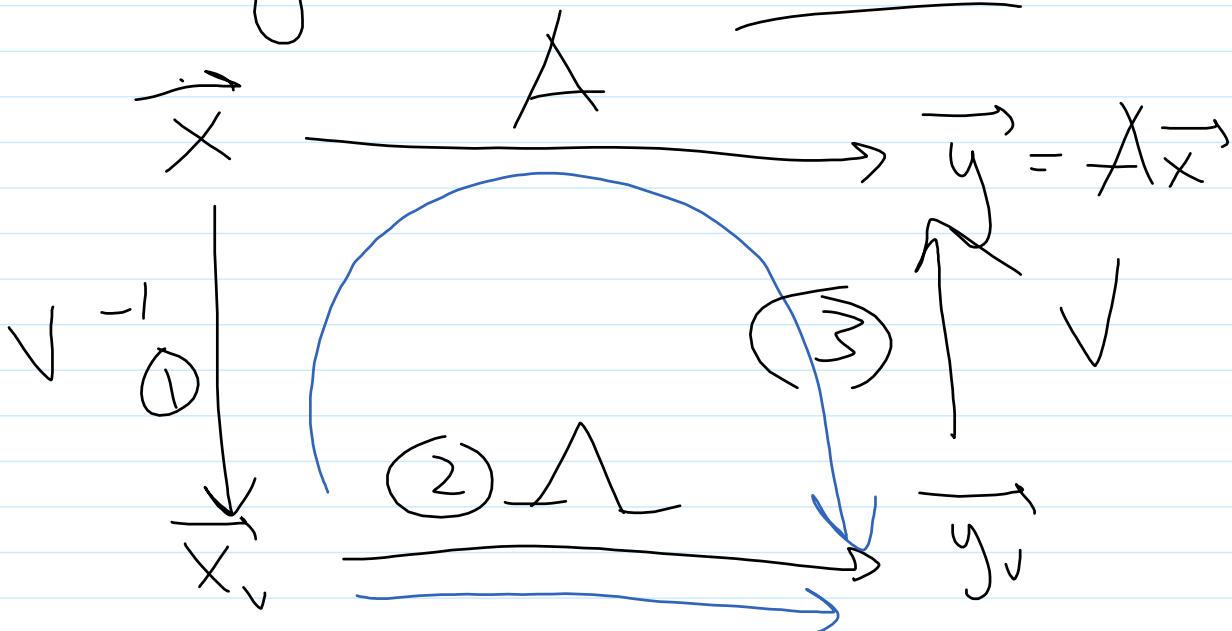II. Diagonalization & Change of Basis

$$\vec{y} = A \vec{x} = V \Lambda V^T \vec{x}$$



① Change to eigenbasis - diag

coordinates x_v

② Scale w/ diagonal matrix Λ

③ Transform result back to std basis
 $\vec{y}_v \rightarrow \vec{y}$

$$\text{Step 1: } \vec{x} \xrightarrow{\text{A}} \vec{y}_v \xrightarrow{\text{V}^{-1}} \vec{y}$$

Step 2 in more detail!

$$\begin{aligned} A\vec{x} &= \vec{y} \\ \Delta \vec{x}_v &= \vec{y}_v \end{aligned}$$


very similar
looking...

Suggests that Δ is the representation of A in eigenbasis

\Rightarrow How do we get Δ ?


$$A = V\Delta V^{-1} \Rightarrow \Delta = V^{-1}AV$$

Look at chart:

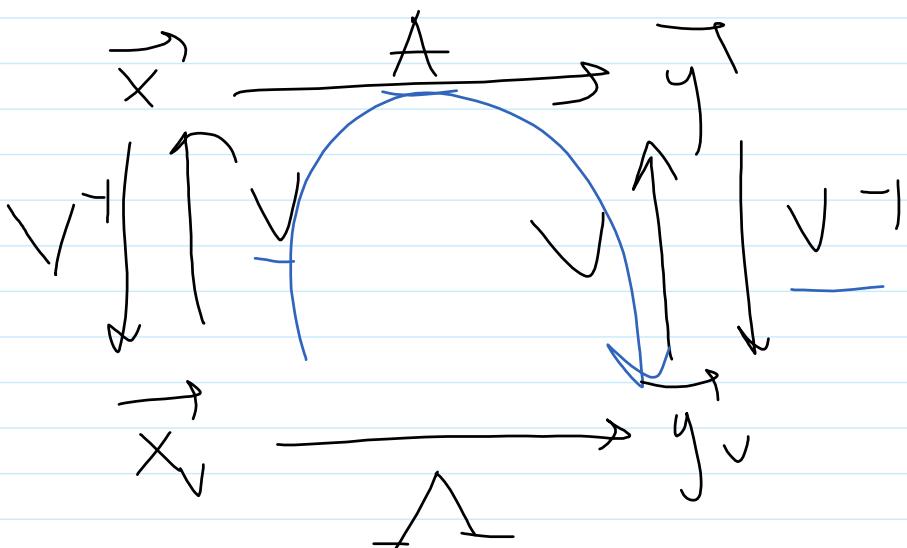

$$\underline{\Lambda} = \underline{V}^{-1} \underline{A} \underline{V}$$

What about other bases?

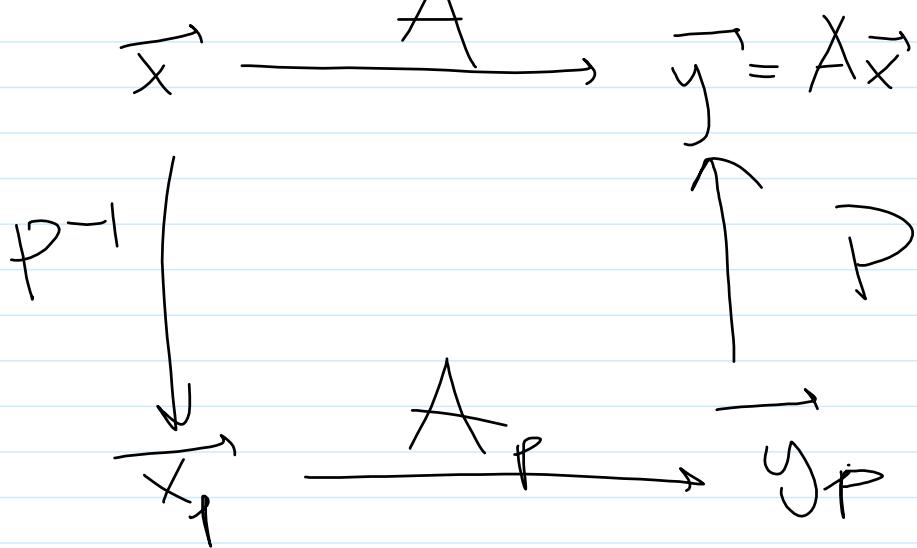

$$\underline{A} = \underline{P} \underline{A}_P \underline{P}^+ \iff \underline{A}_P = \underline{P}^{-1} \underline{A} \underline{P}$$

(also known as a similarity transformation)

III. Circuit Examples of
Matrix Diff Eq


→ See worksheet

Dis 3B Worksheet

Tuesday, July 7, 2020 12:14 AM

1 LC Tank

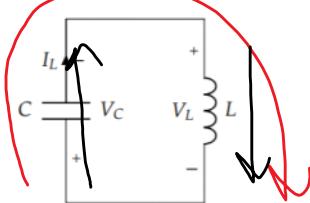Consider the following circuit like you saw in lecture:



This is sometimes called an *LC* tank and we will derive its response in this problem. Assume at $t = 0$ we have $V_C(0) = V_s = 1$ V and $\frac{dV_C}{dt}(t = 0) = 0$. Also suppose $L = 9\text{nH}$ and $C = 1\text{nF}$.

$$\begin{aligned} x_1(t) &= \sqrt{C} \\ x_2(t) &= \frac{1}{\sqrt{L}} \frac{dV_C}{dt} \end{aligned}$$

- a) Write the system of differential equations in terms of state variables $x_1(t) = I_L(t)$ and $x_2(t) = V_C(t)$ that describes this circuit for $t \geq 0$. Leave the system symbolic in terms of V_s , L , and C .

$$x_1(t) = \overline{I}_L(t)$$

$$x_2(t) = \overline{V}_C(t)$$

$$\text{KCL: } \overline{I}_C(t) - \overline{I}_L(t) = x_1(t)$$

$$x_1(t) = C \frac{d\overline{V}_C}{dt} = C \frac{d}{dt} x_2(t)$$

$$\text{KVL: } \overline{V}_C + \overline{V}_L = 0$$

$$x_2(t) = -\overline{V}_L(t) = -L \frac{d\overline{I}_L}{dt} = -L \frac{dx_1}{dt}$$

In sum,

$$x_1(t) = C \frac{d x_2(t)}{dt}$$

$$x_2(+) = -L \frac{d x_1(+)}{dt}$$

b) Write the system of equations in vector/matrix form with the vector state variable

$\vec{x}(t) = \begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix}$. This should be in the form $\frac{d}{dt} \vec{x}(t) = A \vec{x}(t)$ with a 2×2 matrix A .

Find the initial conditions $\vec{x}(0)$.

$$\Rightarrow \begin{bmatrix} \frac{d x_1}{dt} \\ \frac{d x_2}{dt} \end{bmatrix} = \begin{bmatrix} -\frac{1}{L} x_2(+) \\ \frac{1}{C} x_1(+) \end{bmatrix}$$

$$\begin{bmatrix} \frac{d}{dt} \begin{bmatrix} x_1(+) \\ x_2(+) \end{bmatrix} \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & 0 \end{bmatrix} \begin{bmatrix} x_1(+) \\ x_2(+) \end{bmatrix}$$

$$\vec{x}(0) = \begin{bmatrix} I_L(0) \\ V_C(0) \end{bmatrix} = \begin{bmatrix} 0 \\ V_S \end{bmatrix}$$

c) Find the eigenvalues of the A matrix symbolically.

$$\det \left[A - \lambda I \right] = \det \begin{bmatrix} -\lambda & -\frac{1}{L} \\ \frac{1}{C} & -\lambda \end{bmatrix} = 0$$

$$\lambda^2 - \left(-\frac{1}{LC} \right) = \lambda^2 + \frac{1}{LC} = 0$$

$$\lambda = \pm \frac{j}{\sqrt{LC}}$$

d) Recall from yesterday's discussion that solutions for $x_i(t)$ will all be of the form

$$x_i(t) = \sum_k c_k e^{\lambda_k t}$$

where λ_k is an eigenvalue of our differential equation relation matrix A . Thus, we make the following guess for $\vec{x}(t)$:

$$\begin{bmatrix} x_1(t) \\ x_2(t) \end{bmatrix} = \begin{bmatrix} c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t} \\ c_3 e^{\lambda_1 t} + c_4 e^{\lambda_2 t} \end{bmatrix}$$

where c_1, c_2, c_3, c_4 are all constants.

Evaluate $\vec{x}(t)$ and $\frac{d\vec{x}}{dt}(t)$ at time $t = 0$ in order to obtain four equations in four unknowns.

4 unknowns \rightarrow 4 lin. ind. eqns

$$\vec{x}(0) = \begin{bmatrix} 0 \\ \sqrt{s} \end{bmatrix} = \begin{bmatrix} c_1 e^{\lambda_1 0} + c_2 e^{\lambda_2 0} \\ c_3 e^{\lambda_1 0} + c_4 e^{\lambda_2 0} \end{bmatrix} \Big|_{t=0}$$

$$\begin{bmatrix} 0 \\ \sqrt{s} \end{bmatrix} = \begin{bmatrix} c_1 + c_2 \\ c_3 + c_4 \end{bmatrix}$$

$$\frac{d\vec{x}}{dt} = \begin{bmatrix} c_1 \lambda_1 e^{\lambda_1 t} + c_2 \lambda_2 e^{\lambda_2 t} \\ c_3 \lambda_1 e^{\lambda_1 t} + c_4 \lambda_2 e^{\lambda_2 t} \end{bmatrix} \Big|_{t=0}$$

$$= A \vec{x} = \begin{bmatrix} -\frac{1}{L} x_2(+) \\ \frac{1}{C} x_1(+) \end{bmatrix} \Big|_{t=\lambda}$$

$$\left[\begin{array}{c} c_1 x_1(+) \\ c_2 x_2(+) \\ c_3 x_1(-) \\ c_4 x_2(-) \end{array} \right] = \left[\begin{array}{c} -\frac{1}{L} x_2(+) \\ \frac{1}{C} x_1(+) \\ -\frac{V_s}{L} \\ 0 \end{array} \right]$$

e) Solve those equations for c_1, c_2, c_3, c_4 and plug them into your guess for $\vec{x}(t)$. What do you notice about the solutions? Are they complex functions? HINT: Remember $e^{j\theta} = \cos(\theta) + j \sin(\theta)$.

$$c_1 = -\sqrt{\frac{C}{L}} \frac{V_s}{2j}$$

$$c_2 = \sqrt{\frac{C}{L}} \frac{V_s}{2j}$$

$$c_3 = c_4 = \frac{V_s}{2}$$

$$x_1(+) = -\sqrt{\frac{C}{L}} \frac{V_s}{2j} e^{\frac{j}{\sqrt{LC}} t} + \sqrt{\frac{C}{L}} \frac{V_s}{2j} e^{-\frac{j}{\sqrt{LC}} t} +$$

$$= -\sqrt{\frac{C}{L}} \left(\frac{e^{\frac{j}{\sqrt{LC}} t} - e^{-\frac{j}{\sqrt{LC}} t}}{2j} \right)$$

$$x_1(+) = \bar{x}_1(t) = -\sqrt{\frac{C}{L}} V_s \sin \left(\frac{1}{\sqrt{LC}} t \right)$$

$$X_L(t) = \frac{1}{L}(t) = -\frac{1}{L} \bar{V}_s \sin(\sqrt{LC}\tau)$$

$$V_L(t) = \frac{\bar{V}_s}{2} \left[e^{\frac{j}{\sqrt{LC}}t} + e^{-\frac{j}{\sqrt{LC}}t} \right]$$

$$V_C(t) = \bar{V}_s \cos\left(\frac{1}{\sqrt{LC}}t\right)$$

$$L = 9 \text{ nH}, C = 1 \text{ nF}$$


$$\frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-9} \times 9 \times 10^{-9}}} = \frac{1}{3 \text{ ns}}$$


$$\sqrt{\frac{C}{L}} = \sqrt{\frac{1 \text{ nF}}{9 \text{ nH}}} = \frac{1}{3}$$

$$\bar{V}_s = 1 \text{ V}$$

$$I_L(t) = -\frac{1}{3} \sin\left(\frac{t}{3 \text{ ns}}\right) \text{ [A]}$$

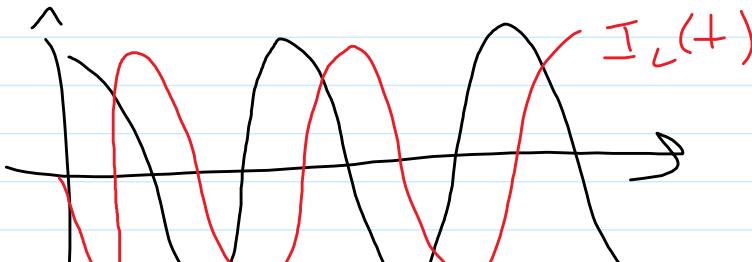
$$V_C(t) = \cos\left(\frac{t}{3 \text{ ns}}\right) \text{ [V]}$$



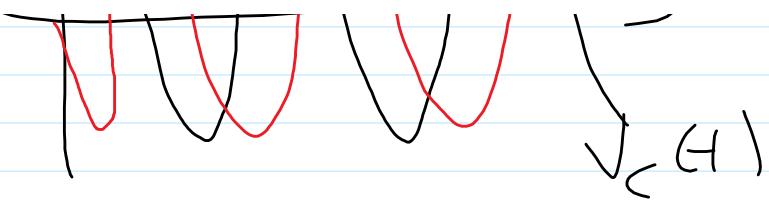


$$U_c = \frac{1}{2} C V_c^2 \propto \cos^2\left(\frac{t}{3_{rs}}\right)$$
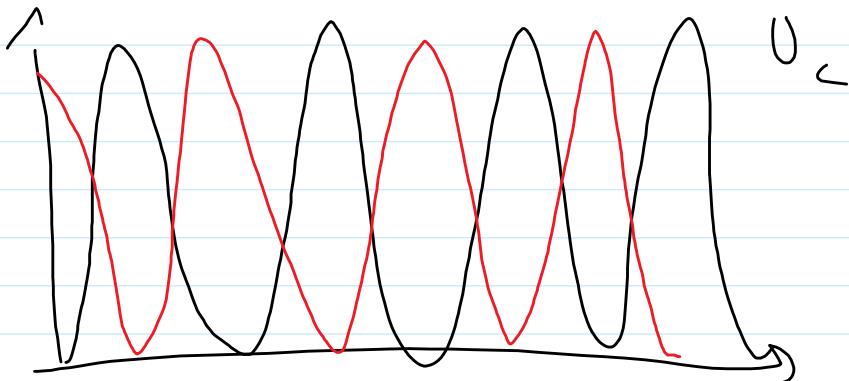
$$U_L = \frac{1}{2} L I_L^2 \propto \sin^2\left(\frac{t}{3_{rs}}\right)$$



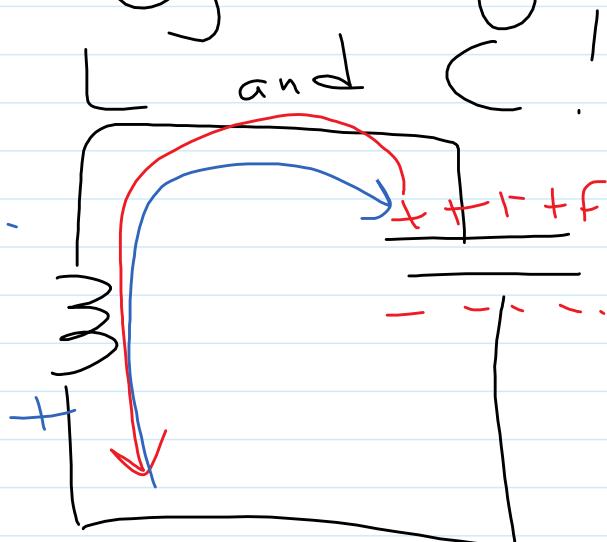Energy oscillating back and forth \downarrow



① C discharges, current flows through L

② L builds up voltage b/c of changing current

③ this voltage pushes charge back onto C

Mathematically,



Mathematically,
same as STHO!
back onto 0C



$$F = -kx$$


$$I_L(t) = C \frac{dV_C}{dt} \stackrel{\text{---}}{=} -LC \frac{\frac{dI_L}{dt}}{\text{---}} \stackrel{\text{---}}{=}$$
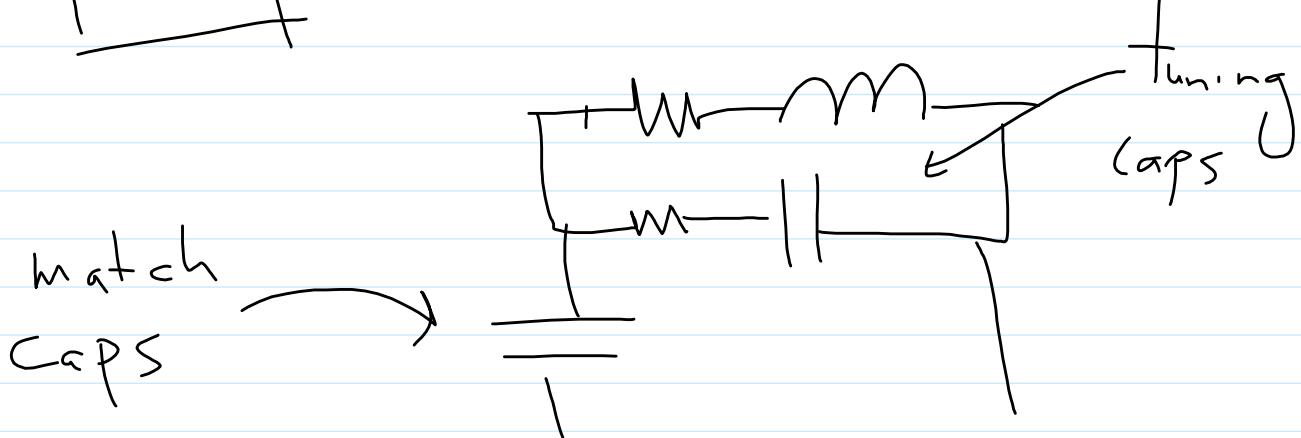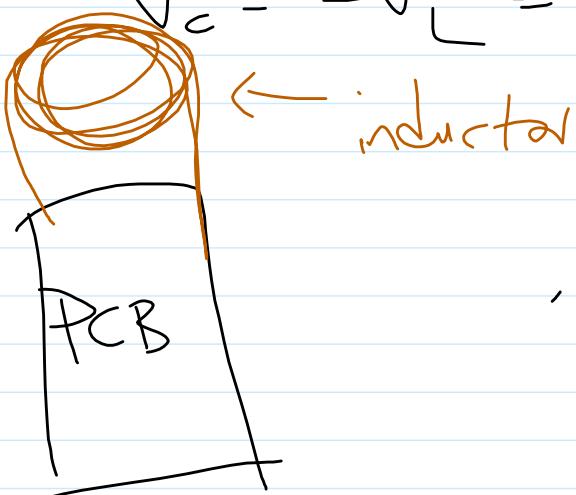
$$V_C = -V_L = -L \frac{dI_L}{dt} \stackrel{\text{---}}{=}$$




2 Charging RLC Circuit

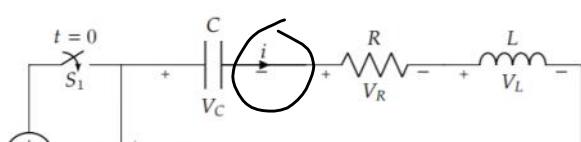Consider the following circuit. Before $t = 0$, switch S_1 is off while S_2 is on. At $t = 0$, both switches flip state (S_1 turns on and S_2 turns off):



$$V_s = V_s$$

$$V_- = 0$$

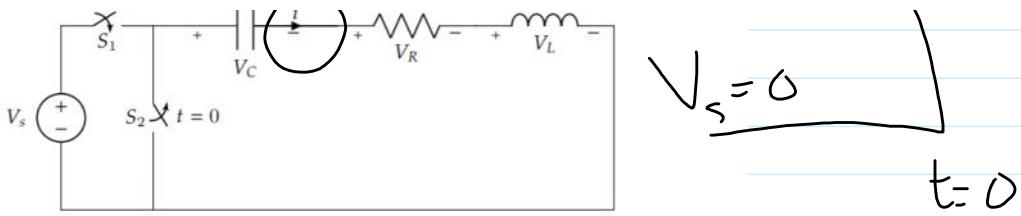

$$V_s = 0$$

$t=0$

a) Write out the differential equation describing this circuit for $t \geq 0$ in the form:

$$\frac{d^2 V_c}{dt^2} + a_1 \frac{d V_c}{dt} + a_0 V_c = b$$

$$V_s = V_c + V_R + V_L = V_c + iR + L \frac{di}{dt}$$

$$i = C \frac{dV_c}{dt}$$

$$\Rightarrow V_s = V_c + RC \frac{dV_c}{dt} + LC \frac{d^2 V_c}{dt^2}$$

$$\frac{d^2 V_c}{dt^2} + \frac{R}{L} \frac{dV_c}{dt} + \frac{1}{LC} V_c = \frac{V_s}{LC}$$

b) Find a \tilde{V}_c and substitute it to the previous equation such that

$$\frac{d^2 \tilde{V}_c}{dt^2} + a_1 \frac{d \tilde{V}_c}{dt} + a_0 \tilde{V}_c = 0$$

$$\tilde{V}_c = V_c - V_s$$

$$\frac{d \tilde{V}_c}{dt} = \frac{d V_c}{dt}$$

$$\frac{d \tilde{V}_c}{dt} = \frac{d V_c}{dt} - \cancel{\frac{d V_s}{dt}}$$

$$\frac{d^2 \tilde{V}_c}{dt^2} = \frac{d^2 V_c}{dt^2}$$

$$\frac{d^2 \tilde{V}_c}{dt^2} + \frac{R}{L} \frac{d \tilde{V}_c}{dt} + \frac{1}{LC} (\tilde{V}_c) = \frac{1}{LC} (V_s)$$

$$\frac{d^2 \tilde{V}_c}{dt^2} + \frac{R}{L} \frac{d\tilde{V}_c}{dt} + \frac{1}{LC} (\tilde{V}_c - V_s) = 0$$

$$\boxed{\frac{d^2 \tilde{V}_c}{dt^2} + \frac{R}{L} \frac{d\tilde{V}_c}{dt} + \frac{1}{LC} \tilde{V}_c = 0}$$

$$\Rightarrow \frac{d^2 \tilde{V}_c}{dt^2} = -\frac{1}{LC} \tilde{V}_c - \frac{R}{L} \frac{d\tilde{V}_c}{dt}$$

c) Solve for $\tilde{V}_c(t)$ for $t \geq 0$. Use component values $V_s = 4V$, $C = 2fF$, $R = 60k\Omega$, and $L = 1\mu H$.

$$X_1(+) = \tilde{V}_c$$

$$X_2(+) = \frac{d\tilde{V}_c}{dt}$$

$$\frac{d}{dt} \left[\begin{bmatrix} \tilde{V}_c \\ \frac{d\tilde{V}_c}{dt} \end{bmatrix} \right] = \left[\begin{bmatrix} \frac{d\tilde{V}_c}{dt} \\ -\frac{1}{LC} \tilde{V}_c - \frac{R}{L} \frac{d\tilde{V}_c}{dt} \end{bmatrix} \right]$$

$$= \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} \tilde{V}_c \\ \frac{d\tilde{V}_c}{dt} \end{bmatrix}$$

$$\det \begin{bmatrix} -\lambda & 1 \\ -\frac{1}{LC} & -\lambda - \frac{R}{L} \end{bmatrix} = 0$$

$$\Rightarrow \lambda\left(\lambda + \frac{R}{L}\right) + \frac{1}{LC} = 0$$

$$\lambda^2 + \frac{R}{L}\lambda + \frac{1}{LC} = 0$$

$$\lambda = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$

$$= -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$R = 60k\Omega \quad C = 2 \text{ fF}$$

$$L = 1 \text{ mH}$$

$$\boxed{\begin{aligned} \lambda_1 &= -1 \times 10^{10} \\ \lambda_2 &= -5 \times 10^{16} \end{aligned}}$$

$$\tilde{V}_C(t) = C_1 e^{\lambda_1 t} + C_2 e^{\lambda_2 t}$$

$$\Rightarrow V_C(t) - V_S = C_1 e^{\lambda_1 t} + C_2 e^{\lambda_2 t}$$

$$V_c(t) = V_s + c_1 e^{d_1 t} + c_2 e^{d_2 t}$$

Initial Conditions:

steady-state:



$$I=0, V=0 \text{ for } t < 0$$

① $I = I_c = C \frac{dV_c}{dt} \leftarrow I_c \text{ can't be } \infty,$
 $\text{So } V_c \text{ cannot change instantaneously}$

 $V_c(t < 0) = 0 \Rightarrow V_c(t = 0) = 0$

$$V_c(0) = 0 = V_s + c_1 e^0 + c_2 e^0$$

$$= V_s + c_1 + c_2$$

② $\frac{dV_c}{dt}(t=0) = ?$

$$\downarrow I_L \quad | \quad \underline{dI_L} \quad | \quad \underline{\Delta I_C}$$

$$V_L = L \frac{dI_L}{dt} = L \frac{\downarrow I_C}{dt}$$

↙ V can't be ∞ , so
current can't change instantaneously
across an inductor

$$\bar{I}_L(t < 0) = \bar{I}_L(t = 0) = 0$$

$$= \bar{I}_C(t = 0) = C \frac{dV_c}{dt}(0)$$

$$\frac{dV_c}{dt}(t = 0) = 0$$

$$\frac{dV_c}{dt} = \frac{d}{dt} \left(V_s + c_1 e^{\lambda_1 t} + c_2 e^{\lambda_2 t} \right)$$

$$t = 0$$

$$0 = c_1 \lambda_1 + c_2 \lambda_2$$

$$\Rightarrow \begin{bmatrix} V_c(0) \\ \frac{dV_c}{dt}(0) \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \quad \text{I.C.'s}$$


$$V_s + c_1 + c_2 = 0$$

$$c_1 \lambda_1 + c_2 \lambda_2 = 0$$

$$\Rightarrow c_1 = -5$$

$$c_2 = 1$$
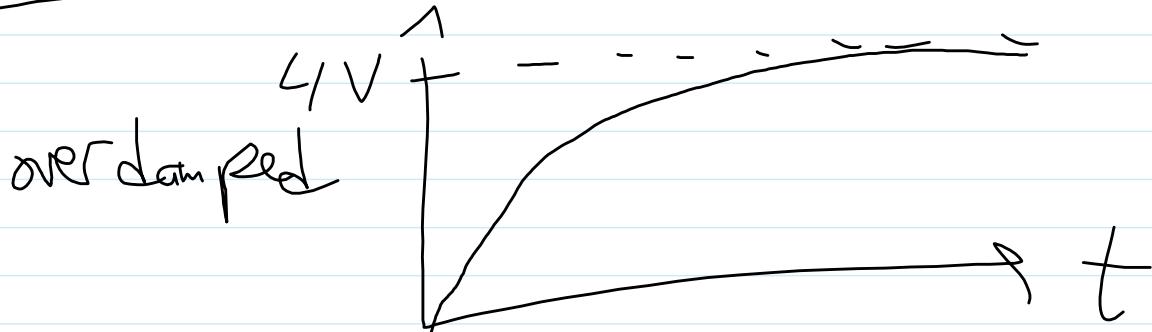
$$V_c(t) = 4 - 5e^{-10^6 t} + e^{-(5 \times 10^{10}) t}$$



$$\lambda = \sigma + j\omega$$

$$e^{(\sigma+j\omega)t} = e^{\sigma t} e^{j\omega t}$$

